
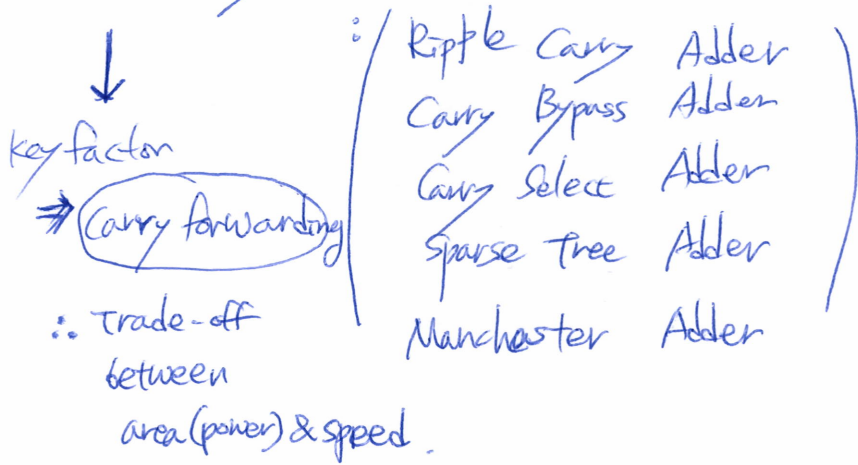


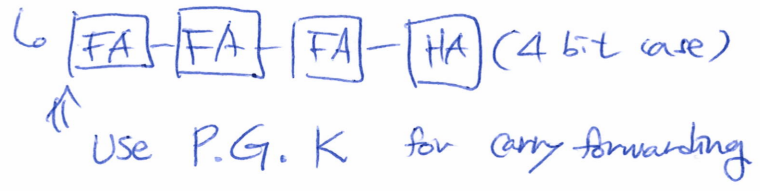* **Adder** - Area & Delay → Depends on structure




Integer Signed 2's complement, unsigned, ...




Fixed Point

(fast addition)

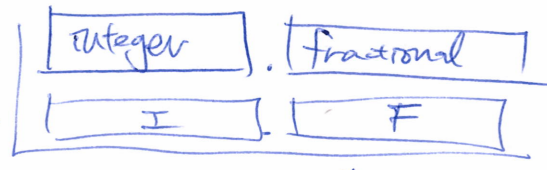


① Just like adding two integers

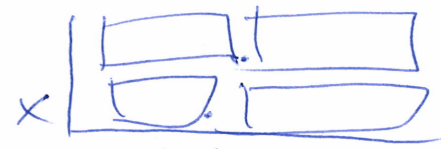


① multiplying 2 integers & consider position of the radix point

Floating point

(fast multiplication)

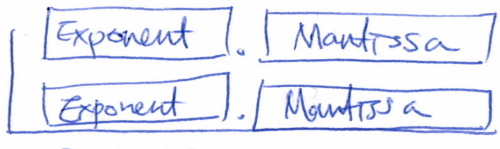

- ① Match exponent
- ② Add Mantissa

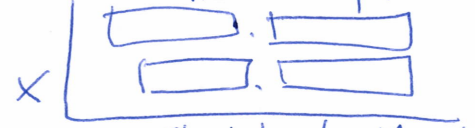


- ① Multiply Mantissas
- ② Add exponents

ex 1.01101×1011





sign 1 bit -127 -128, 8 bits (start from -127) 23 bits ⇒ 32 bits

ALU (Arithmetic Logic Unit)

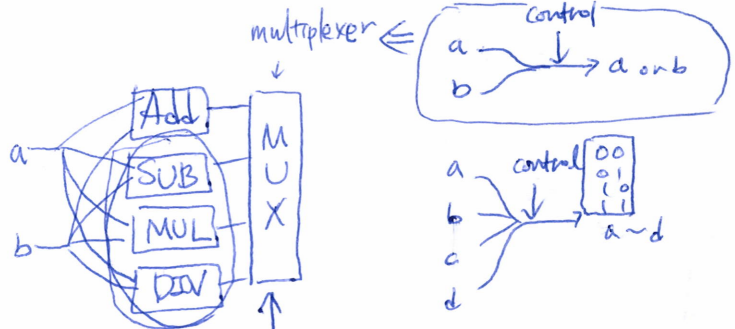

In fact... all arithmetic operation can be done by Adder

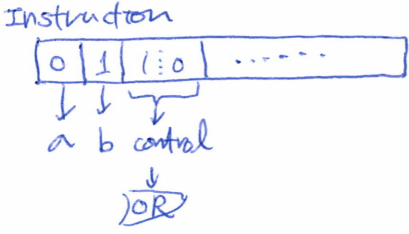
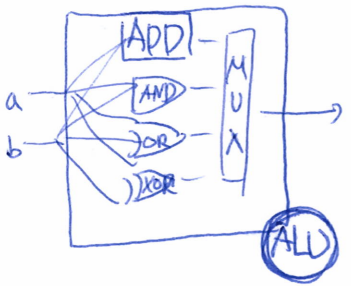
control { 00 (add), 01 (sub), 10 (MUL), 11 (DIV) }




∴ Carry look-ahead !

(goal ; all r_i & c_i are calculated at the same clock!!)


MUL

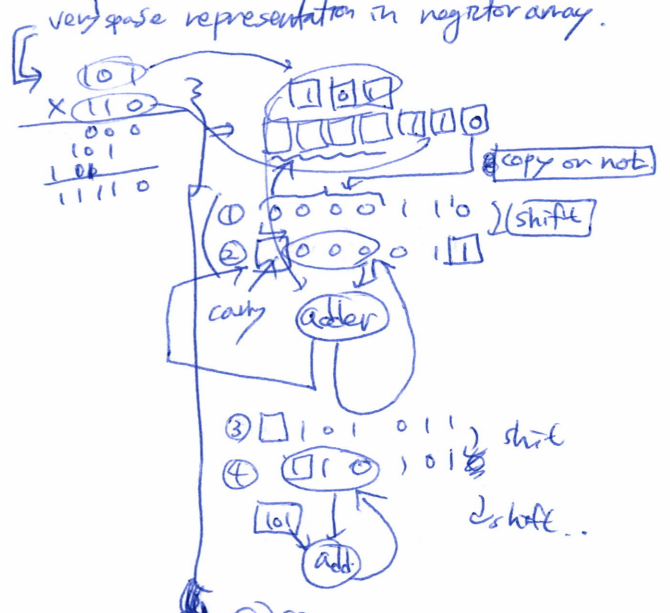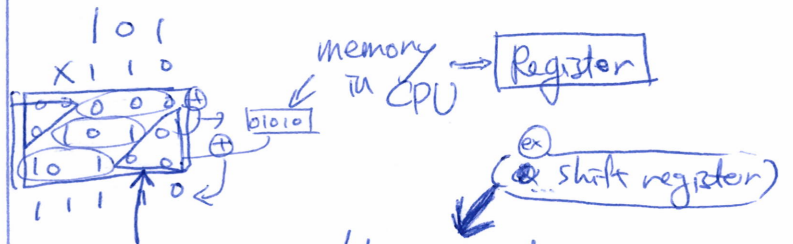


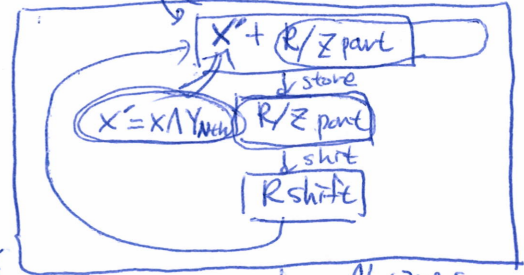
(1) X N-bit upper operand
 (2) Z(N+1) bit storage + N bit lower operand



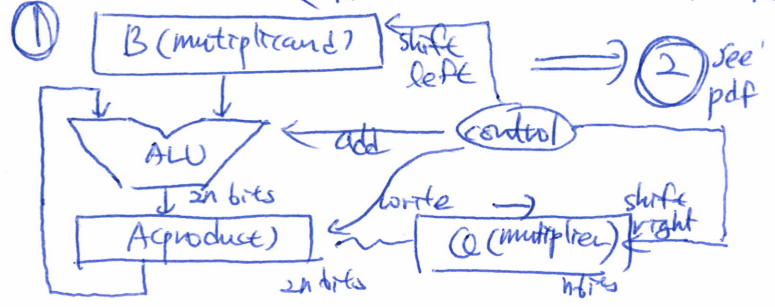original \downarrow N times
 < R = multiplication result ! >



32-bit ALU

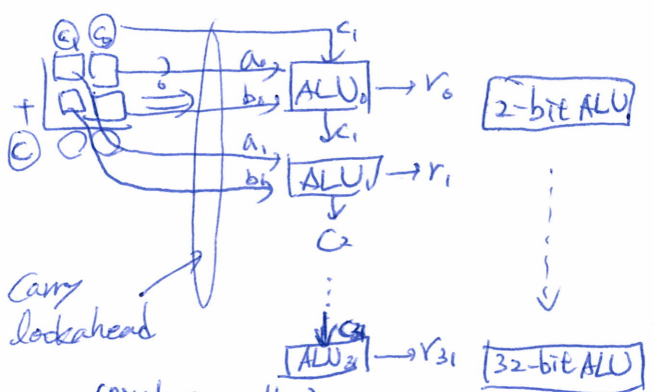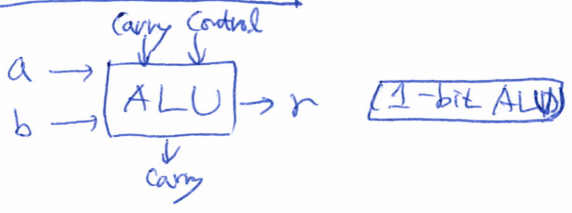

(Ripple carry adder)
 ⇒ This structure needs 32 times (energy/time)